

Pylon Training

1. $S_{out} = A \oplus B \oplus C_{in}$ $C_{out} = (C_{in}(A+B)) + AB$

A	B	C _{in}	S _{out}	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


	AB		S _{out}	
	00	01	11	10
C _{in} 0	0	1	0	1
1	1	0	1	0

	C _{out}		C _{in}	
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$A \oplus B \oplus C_{in}$


$C_{in} \cdot B + (C_{in} \cdot A + AB)$
 $(C_{in}(A+B)) + AB$

Σ.

 

$$A_1 B_1 = 11$$

$$A_0 B_0 = 01$$

 

3a.

3b.

Each adder has 6 gates; 1 xor, 2 and, 1 or

and there's one xor to check the carry, so $2 \times 6 + 1 = 13$ gates

4.

```
module myfulladd(A, B (in, S, (out));
    input A, B, (in);
    output S, (out);
    assign S = (A ^ B ^ (in));
    assign (out) = ((A & B) | ((in & (A | B))));
endmodule
```

5.

```
module myadder2 (A1, A0, B1, B0, (C), S1, S0, (2));
    input A1, A0, B1, B0, (C);
    output S1, S0, (2);
    wire C1;

    myfulladd u0 (A0, B0, (C), S0, (C1));
    myfulladd u1 (A1, B1, (C1), S1, (2));
endmodule
```

6.

All outputs would be 0.

The outputs should just stay the same.

I would make the inputs all work so every carry = 1 to test it.

I'd look at the sum.

By testing all of these cases, I think it would be satisfactory to say the circuit works